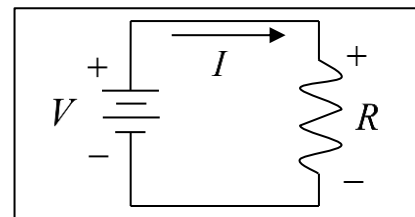


## Elementary Engineering Mathematics

### Application of Lines in Electric Circuits

#### DC Circuit with a Single Resistor

A direct current (DC) circuit with a single resistor is shown in the diagram. The symbol  $V$  represents the applied voltage, the symbol  $R$  represents the resistance of the resistor, and the symbol  $I$  represents the current flowing through the circuit.



Symbol	Description	Units
$V$	Applied voltage (e.g. battery voltage)	volts (V)
$R$	Resistance of resistor	ohms ( $\Omega$ )
$I$	Current passing through the circuit	amps (A)

There are *two important laws* that enable us to relate these three variables, **Ohm's Law** and **Kirchhoff's Voltage Law**.


	Equation	Description
Ohm's Law	$V_R = R I$	The <b>voltage drop across the resistor</b> is the product of its resistance and the current passing through it.
Kirchhoff's Voltage Law	$\sum (\text{voltage rises}) = \sum (\text{voltage drops})$	The sum of voltage rises must equal the sum of the voltage drops around any loop in a circuit.

Applying Kirchhoff's voltage law and Ohm's law to the circuit gives  $V = V_R = R I$ . This is the equation of a line relating the current to the applied voltage. The slope ( $m$ ) of the line is the resistance  $R$ , and the intercept ( $b$ ) is zero.

#### Example #1

Given: For the circuit shown, the following data were measured.

$V$ (volts)	$I$ (amps)
5	0.05
10	0.1

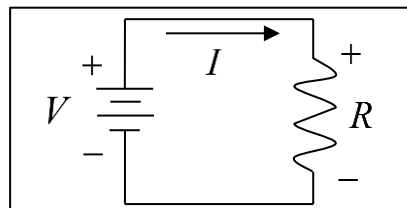

Find: The resistance  $R$ .

Solution:

The **current** is related to the **applied voltage** by the equation  $\boxed{V = RI}$ , so we can find the resistance by finding the slope of the line.

$$\boxed{R = m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{V_2 - V_1}{I_2 - I_1} = \frac{10 - 5}{0.1 - 0.05} = 100 \text{ (ohms, } \Omega \text{)}}$$


So now we have:  $\boxed{V = 100 I}$

**Note:** Because the **intercept** is **zero**, we could have used the point  $(x_1, y_1) = (0, 0)$  with either of the data values given.

Example #2

Given: In the circuit shown,  $V$  is a **known** constant voltage source and  $V_u$  is an **unknown** constant voltage source. For the circuit shown, the following data were measured.

$V$ (volts)	$I$ (amps)
15	0.03333
30	0.1333

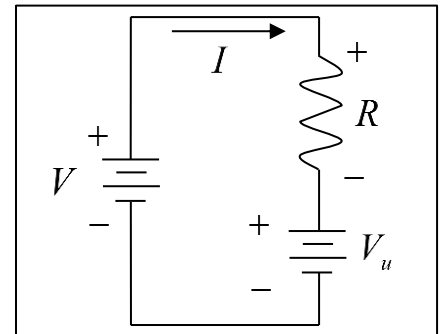

Find: The resistance  $R$  and the unknown voltage source  $V_u$ .

Solution:

Applying Kirchhoff's voltage law to this circuit gives  $\boxed{V = V_R + V_u = RI + V_u}$ . So, the resistance  $R$  is the **slope** (as before), and the unknown voltage  $V_u$  is the **intercept**.


$$\boxed{R = m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{V_2 - V_1}{I_2 - I_1} = \frac{30 - 15}{0.1333 - 0.03333} = 150.05 \approx 150 \text{ (}\Omega\text{)}}$$

So now we have:  $\boxed{V = 150 I + V_u}$

To find the intercept, we use this result with **either** of the two data points.

$$\boxed{V_u = V - 150 I = \begin{cases} 15 - (150 \times 0.03333) = 10.0005 \approx 10 \text{ (volts)} \\ \text{or} \\ 30 - (150 \times 0.1333) = 10.005 \approx 10 \text{ (volts)} \end{cases}}$$

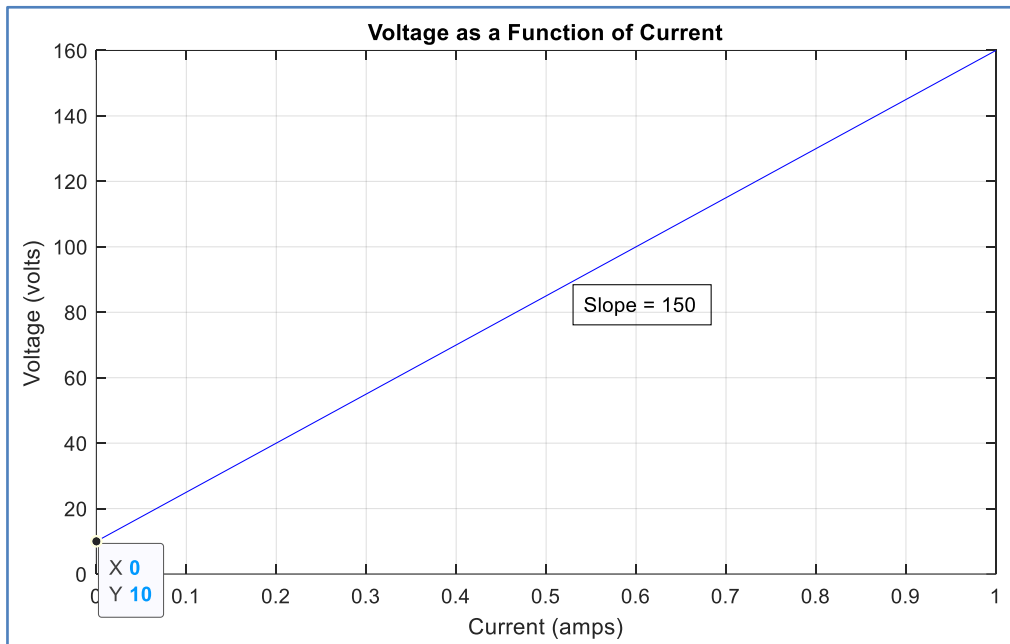We now have the completed equation:  $\boxed{V = 150 I + 10}$



### Example #3

In the above examples, the **current**  $I$  is the **independent** variable and the **voltage**  $V$  is the **dependent** variable. We can easily reverse these roles by solving the completed equation for the current  $I$  as a function of the voltage  $V$ .

$$V = 150I + 10 \Rightarrow 150I = V - 10 \Rightarrow I = \left(\frac{1}{150}\right)V - \left(\frac{10}{150}\right) \approx \left(\frac{1}{150}\right)V - 0.0666667$$

