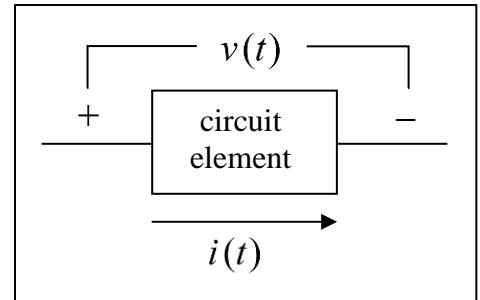


## Elementary Engineering Mathematics

### Application of Derivatives in Electrical Engineering

The diagram shows a typical element (resistor, capacitor, inductor, etc.) in an electrical circuit. Here,  $v(t)$  represents the voltage across the element, and  $i(t)$  represents the current flowing through the element. Both generally are functions of time,  $t$ . For any such element, the following equations apply.



$$\boxed{v(t) = \frac{dw}{dq}} \quad \begin{cases} v(t) \text{ is the voltage (volts)} \\ w(t) \text{ is the energy (joules)} \\ q(t) \text{ is the charge (coulombs)} \end{cases}$$

$$\boxed{i(t) = \frac{dq}{dt}} \quad \begin{cases} i(t) \text{ is the current (amps)} \\ t \text{ is the time (sec)} \end{cases}$$

$$\boxed{p(t) = \frac{dw}{dt} = \left(\frac{dw}{dq}\right)\left(\frac{dq}{dt}\right) = v(t) \cdot i(t)} \quad \{p(t) \text{ is the power (joules/sec) or (watts)}\}$$

This last equation is an application of the **chain rule**.

#### Example 1:

Given: The **charge** and **voltage** for a given circuit element are given by the following equations:

$$\boxed{q(t) = \frac{1}{50} \sin(250\pi t) \text{ (coulombs)}} \quad \text{and} \quad \boxed{v(t) = 100 \sin(250\pi t) \text{ (volts)}}$$

Find: a)  $i(t)$  the **current** passing through the element, b)  $p(t)$  the **power** dissipated by the element, and c)  $p_{\max}$  the **maximum power** dissipated by the element.

#### Solution:


$$\text{a) } i(t) = \frac{dq}{dt} = \frac{d}{dt} \left( \frac{1}{50} \sin(250\pi t) \right) = \frac{1}{50} \times \cos(250\pi t) \times 250\pi = \boxed{5\pi \cos(250\pi t) \text{ (amps)}}$$

$$\begin{aligned} \text{b) } p(t) &= v(t) \cdot i(t) = (100 \sin(250\pi t)) (5\pi \cos(250\pi t)) \\ &= \boxed{500\pi \sin(250\pi t) \cos(250\pi t) \text{ (watts)}} \end{aligned}$$

$$\text{c) To find maximum power, we use the } \textbf{trigonometric identity: } \boxed{2 \sin(\theta) \cos(\theta) = \sin(2\theta)}$$

$$p(t) = 500\pi \sin(250\pi t) \cos(250\pi t) = \frac{1}{2} (500\pi \sin(500\pi t)) = \boxed{250\pi \sin(500\pi t) \text{ (watts)}}$$

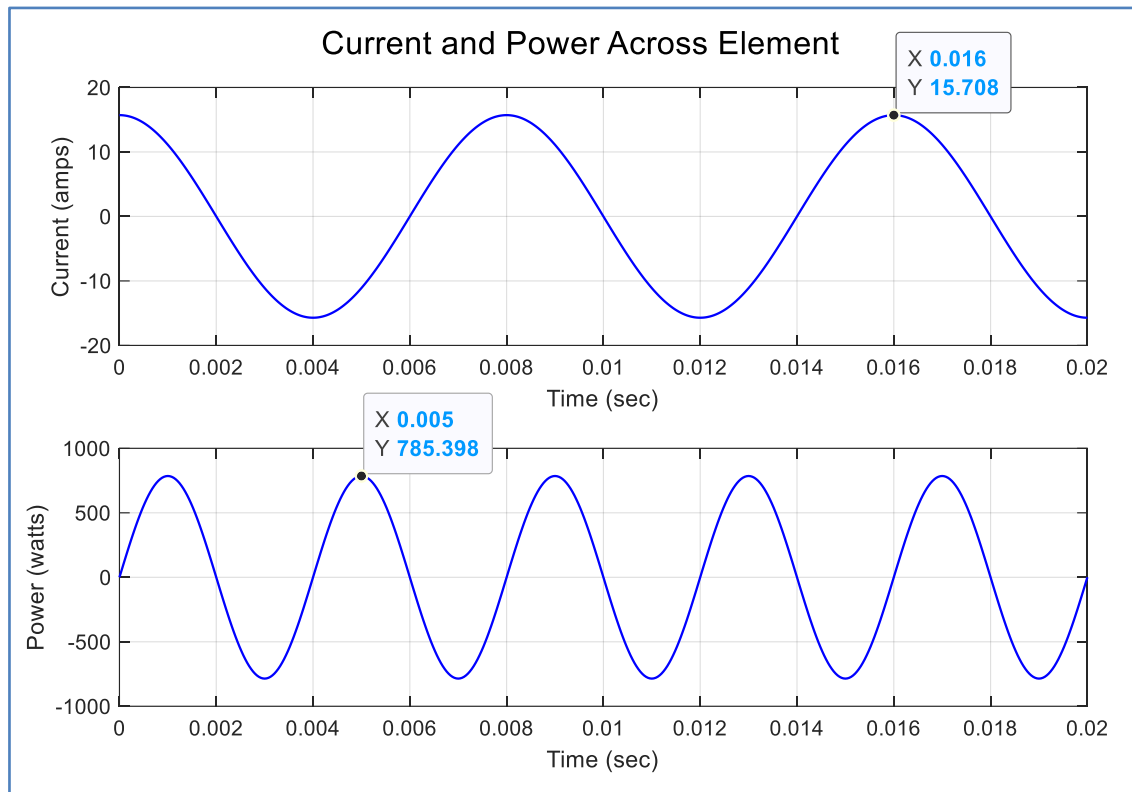
$$\Rightarrow \boxed{p_{\max} = 250\pi \approx 785 \text{ (watts)}}$$


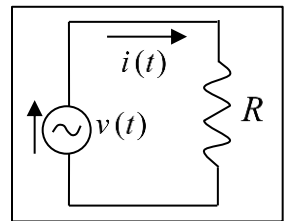
## Current–Voltage Relationships for Resistors, Capacitors, and Inductors


The voltage across and the current through a *resistor* are related simply by its resistance.

$$\boxed{v(t) = Ri(t)} \quad \text{or} \quad \boxed{i(t) = v(t)/R}$$




Given a voltage  $v(t)$  applied to a *capacitor*, the corresponding current  $i(t)$  can be calculated as

$$\boxed{i(t) = C \frac{dv}{dt}}$$

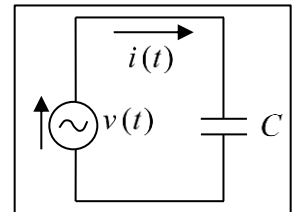

Given the current  $i(t)$  passing through an *inductor*, the corresponding voltage  $v(t)$  can be calculated as


$$\boxed{v(t) = L \frac{di}{dt}}$$

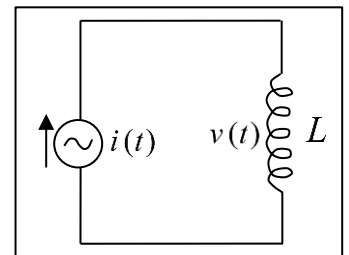

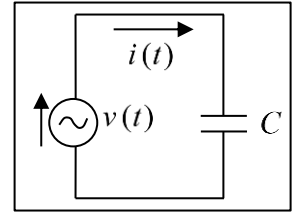Example 2:

Given: A voltage  $v(t) = 110\cos(120\pi t)$  (volts) is applied to a capacitor with  $C = 100$  ( $\mu\text{f}$ ).

Find: a)  $i(t)$  the current through the capacitor, and b)  $p_{\max}$  the maximum power.



Solution:

a) The current can be found by differentiating the voltage.

$$\begin{aligned} i(t) &= C \frac{dv}{dt} = (100 \times 10^{-6}) \frac{d}{dt} (110 \cos(120\pi t)) \\ &= (100 \times 10^{-6}) (110) (120\pi) (-\sin(120\pi t)) \\ &= \boxed{-4.147 \sin(120\pi t) \text{ (amps)}} \end{aligned}$$

$$\begin{aligned} \text{b) } p(t) &= v(t) \cdot i(t) = (110 \cos(120\pi t)) (-4.147 \sin(120\pi t)) \\ &= -456 \sin(120\pi t) \cos(120\pi t) \\ &= -456 \times \frac{1}{2} \sin(240\pi t) \\ &= \boxed{-228 \sin(240\pi t) \text{ (watts)}} \Rightarrow \boxed{p_{\max} = 228 \text{ (watts)}} \end{aligned}$$

Alternate Solution for part (a): (without using derivatives)

We could have solved this problem using **complex numbers**.


$$\begin{aligned} Z_C &= -j/\omega C = -j/(120\pi)(100 \times 10^{-6}) = -j(10^6)/(120\pi)(100) \\ &\approx -j26.526 \text{ (ohms)} \approx 26.526 \angle (-90^\circ) \end{aligned}$$

$$\boxed{I \approx \frac{110 \angle (0^\circ)}{26.526 \angle (-90^\circ)} \approx 4.147 \angle (90^\circ)}$$

$$\Rightarrow i(t) \approx 4.147 \cos(120\pi t + 90^\circ) \text{ (amps)}$$

$$\approx 4.147 \left( \cos(120\pi t) \underbrace{\cos(90^\circ)}_0 - \sin(120\pi t) \underbrace{\sin(90^\circ)}_1 \right)$$
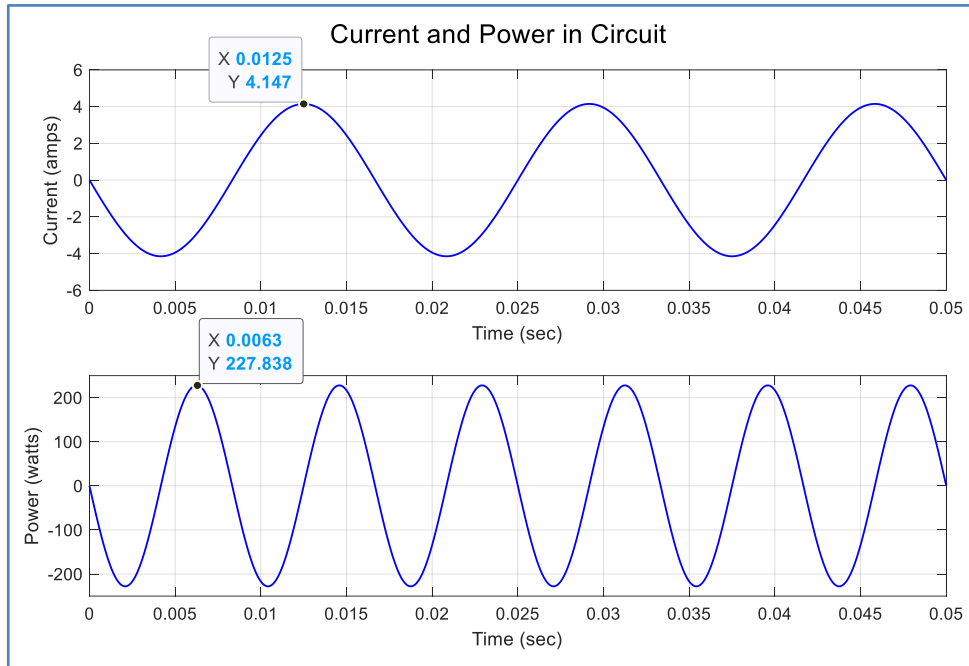
$$\Rightarrow \boxed{i(t) \approx -4.147 \sin(120\pi t) \text{ (amps)}}$$




### Example 3:

Given: A voltage  $v(t) = 110e^{-10t} \cos(120\pi t)$  (volts) is applied to a capacitor with  $C = 100 \text{ } (\mu\text{f})$ .

Find:  $i(t)$ , the current through the capacitor

Solution:

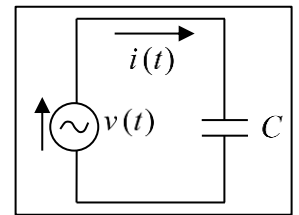

To find the current we differentiate the voltage using the product and chain rules.

$$\begin{aligned}
 i(t) &= C \frac{dv}{dt} = (100 \times 10^{-6}) \frac{d}{dt} (110e^{-10t} \cos(120\pi t)) \\
 &= (100 \times 10^{-6})(110) \left[ \left( \frac{d}{dt} (e^{-10t}) \times (\cos(120\pi t)) \right) + \left( (e^{-10t}) \times \frac{d}{dt} (\cos(120\pi t)) \right) \right] \\
 &= 0.011 \left[ (-10e^{-10t} \cos(120\pi t)) + (-120\pi e^{-10t} \sin(120\pi t)) \right] \\
 &\Rightarrow i(t) \approx -0.011e^{-10t} [10\cos(120\pi t) + 120\pi \sin(120\pi t)] \text{ (amps)}
 \end{aligned}$$


The term in square brackets can be reduced to a **single, phase-shifted sine or cosine** function. For example,

$$120\pi \sin(120\pi t) + 10\cos(120\pi t) = M \cos(120\pi t + \phi)$$

where

$$M = \sqrt{(120\pi)^2 + 10^2} \approx 377.1 \text{ and } \phi = \tan^{-1}(-120\pi / 10) = -88.48^\circ = -1.544 \text{ (rad)}.$$
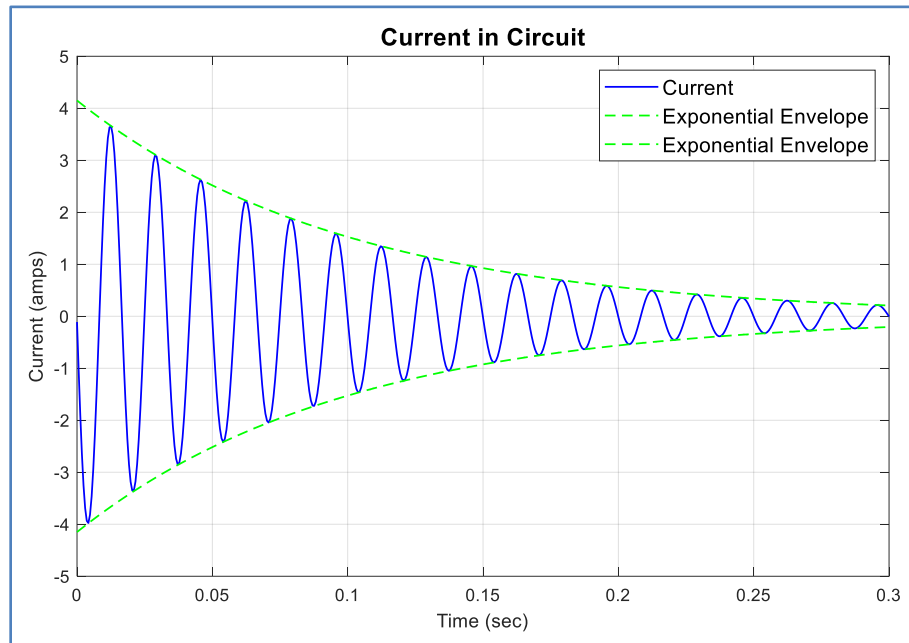
$$\Rightarrow i(t) \approx -4.15e^{-10t} \cos(120\pi t - 1.544) \text{ (amps)}$$



#### Example 4:

Given: Current  $i(t) = 5te^{-10t}$  (amps) is applied to an inductor with  $L = 250$  (mh).

Find:  $v(t)$ , the voltage across the inductor.

Solution:

To find the voltage, we differentiate the current using the product and chain rules.

$$\begin{aligned}
 v(t) &= L \frac{di}{dt} = 0.25 \frac{d}{dt} (5te^{-10t}) = \frac{1}{4} \left( \frac{d}{dt} (5t) \right) (e^{-10t}) + \frac{1}{4} \left( (5t) \frac{d}{dt} (e^{-10t}) \right) \\
 &= \frac{1}{4} (5e^{-10t}) + \frac{1}{4} (5t(-10e^{-10t})) = \frac{1}{4} (5e^{-10t} - 50te^{-10t}) \\
 \Rightarrow v(t) &= \frac{5}{4} e^{-10t} (1 - 10t) \text{ (volts)}
 \end{aligned}$$

