
## **Elementary Engineering Mathematics**


## Exercises #2 – Quadratic Equations

1. A ball is thrown off a tower at a height of 60 (ft) at a speed of 50 (ft/s) and strikes the hill at some point (x, y) as shown. The X and Y positions of the ball are given as functions of time.

$$x(t) = 30t$$
 (ft)  $y(t) = 60 + 40t - 16.1t^2$  (ft)

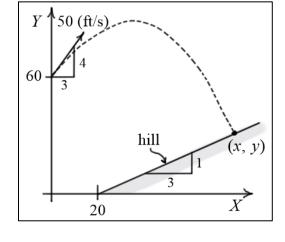- (a) By using the quadratic formula and completing the square, find the times when y = 65 (ft); (b) Find  $y_{\text{max}}$  the maximum height of the ball; (c) By eliminating t from the equations, find y(x);
- (d) Find the equation for the line representing the hill; and
- (e) Find the point where the ball strikes the hill.
- 2. A beam of length L=10 (ft) is cantilevered into a wall. It is subjected to a constant upward distributed load of w = 100 (lb/ft). As a result of this load, the internal bending moment in the beam is found to be a function of x.



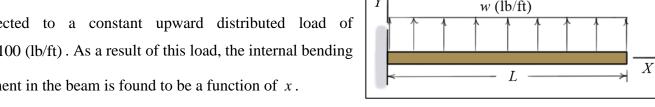

$$M(x) = \frac{1}{2}wx^2 - wLx + \frac{1}{2}wL^2 = 50x^2 - 1000x + 5000 \text{ (ft-lb)}$$

- (a) Find the moments at the ends of the beam, x = 0 and x = L; (b) By using the quadratic formula and completing the square, find the X coordinates of the points where M = 1000 (ft-lb); (c) Find the location and value of the maximum bending moment in the beam; and (d) Convert the maximum bending moment to Newton-meters (N-m).
- 3. The power P supplied to a single-loop circuit can be written as follows:  $\overline{P = RI^2 + VI}$ . Given R = 8 (ohms), V = 16 (volts) and P = 64 (watts), find the current I by (a) factoring, (b) completing the square, and (c) the quadratic formula.
- 4. In the circuit shown, the single equivalent resistance for the three resistors  $R_1$ ,  $R_2$  and  $R_3$  is  $\left| R_{eq} = \left( \frac{R_1 R_2}{R_1 + R_2} \right) + R_3 \right|$ . Given  $R_{eq} = 20$  (ohms),  $R_2 = R_1 - 5$ , and  $R_3 = R_1 + 8$ , find the values of the resistors  $R_1$ ,  $R_2$  and  $R_3$ .

