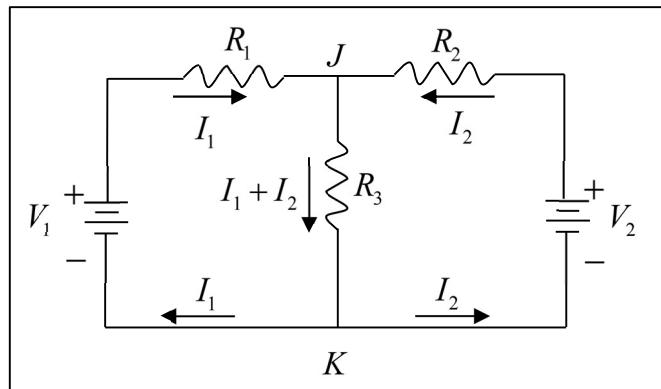


Elementary Engineering Mathematics

Exercises #6 – Two-Dimensional Vectors and Simultaneous Equations



1. For the double-loop DC circuit shown, the currents I_1 and I_2 can be found by solving the following simultaneous equations.

$$\begin{aligned} (R_1 + R_3)I_1 + (R_3)I_2 &= V_1 \\ (R_3)I_1 + (R_2 + R_3)I_2 &= V_2 \end{aligned}$$




Given the resistances $R_1 = 8(\Omega)$, $R_2 = 10(\Omega)$, and $R_3 = 5(\Omega)$, and the voltages $V_1 = 12$ (volts), and $V_2 = 24$ (volts), find the currents I_1 and I_2 using (a) Gaussian elimination (substitution), (b) Cramer's rule, and (c) matrix inversion. Compare the results.

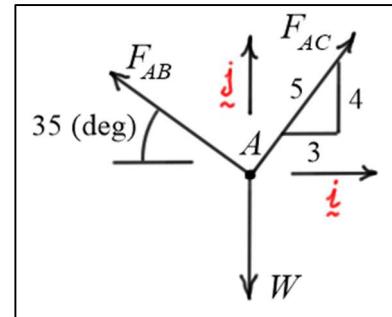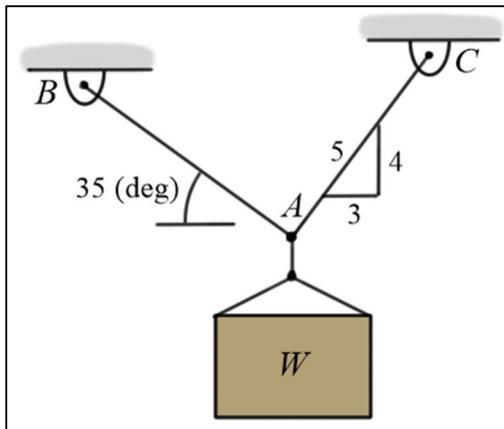2. Given the weight $W = 1000$ (lbs), find F_{AB} and F_{AC} the forces in the supporting wires by setting the sum of the forces to zero at A , using (a) Gaussian elimination (substitution), (b) Cramer's rule, and (c) matrix inversion. Compare the results.



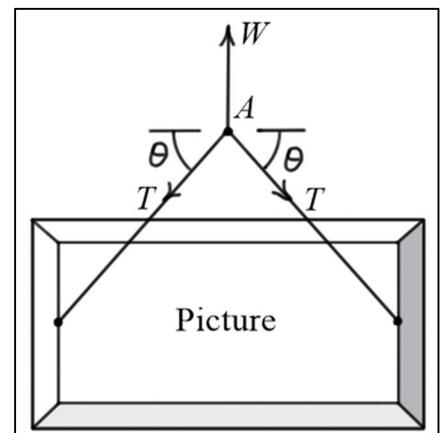3. The figure shows a picture hanging on a wall at point A . The weight of the picture is W . Assuming the picture wire is aligned symmetrically (at an angle θ to the horizontal), find the tension T in the wire as a function of the weight W and angle θ . How does the tension change as the picture wire is shortened, moving A closer to the picture frame? What is the limiting value of T ?



4. The diagram shows a simple truss that is connected to the ground with a pin support at A and a pin and roller support at C . Free body diagrams of the truss and the pin at B are also shown. Using the free body diagram of the **truss**, find (a) the moment of the force \underline{P} about point A , (b) the force \underline{C} so the sum of the moments of forces \underline{A} , \underline{P} , and \underline{C} about A is zero, and (c) the X and Y components of the force \underline{A} so the sum of the forces \underline{A} , \underline{P} , and \underline{C} is zero. Using the free body diagram of pin B , (d) find a set of simultaneous equations you can solve for the magnitudes of forces F_{AB} and F_{BC} by setting $\underline{P} + \underline{F}_{AB} + \underline{F}_{BC} = \underline{0}$, and (e) solve the simultaneous equations using Cramer's rule.

